

Class: CECS 201, Section 7

Lab: 7


Title: 7 Segment Decoder

Student Name: Barry Joseph Okonoboh

Due Date: 11:59:59 P.M., 23, March 2015

Instructor: Dan Cregg

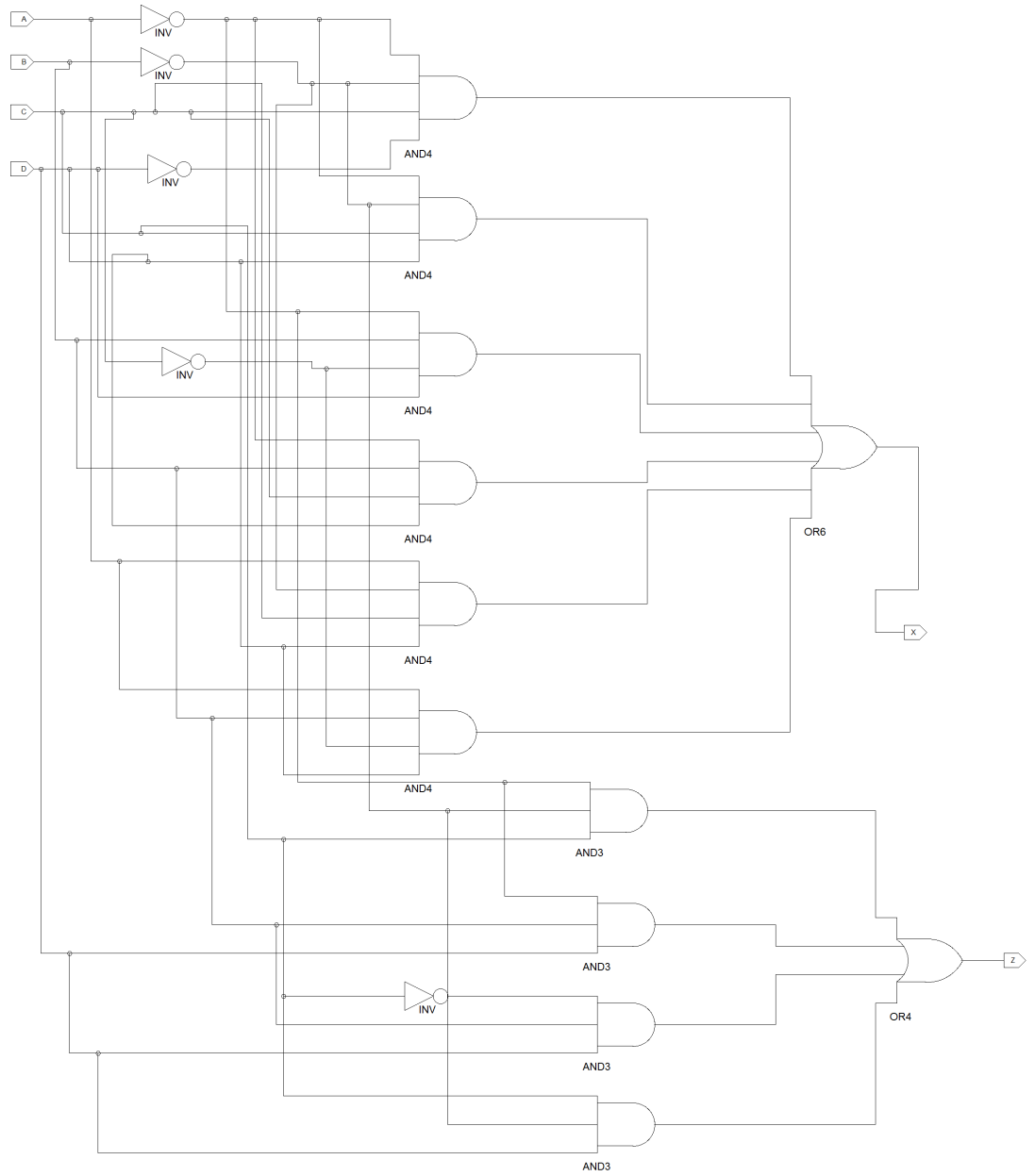- b. **Introduction.** This lab involves using logic gates to determine if a four bit unsigned number is a prime.
- c. **Project Description.** The four bits of the number are mapped to four inputs A , B , C and D . If the number represented by the bits is true, then the output is 1; otherwise, it is 0. A Karnaugh map is used to simplify the equation and both the simplified and unsimplified equations are simultaneously tested using the Diligent board.
- d. **Schematic.**



Truth Table.

A	B	C	D	ledA	ledB	ledC	ledD	ledE	ledF	ledG	ledEnable
0	0	0	0	0	0	0	0	0	0	1	1
0	0	0	1	1	0	0	1	1	1	1	0
0	0	1	0	0	0	1	0	0	1	0	0
0	0	1	1	0	0	0	0	1	1	0	0
0	1	0	0	1	0	0	1	1	0	0	0
0	1	0	1	0	1	0	0	1	0	0	0
0	1	1	0	0	1	0	0	0	0	0	0
0	1	1	1	0	0	0	1	1	1	1	0
1	0	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	1	0	0	0	0
1	0	1	1	1	1	0	0	0	0	0	0
1	1	0	0	0	1	1	0	0	0	1	0
1	1	0	1	1	0	0	0	0	1	0	0
1	1	1	0	0	1	1	0	0	0	0	0
1	1	1	1	0	1	1	1	0	0	0	0