

Class: CECS 201, Section 7

Lab: 6


Title: Logic Word Problem

Student Name: Barry Joseph Okonoboh

Due Date: 07:00:00 P.M., 18, March 2015

Instructor: Dan Cregg

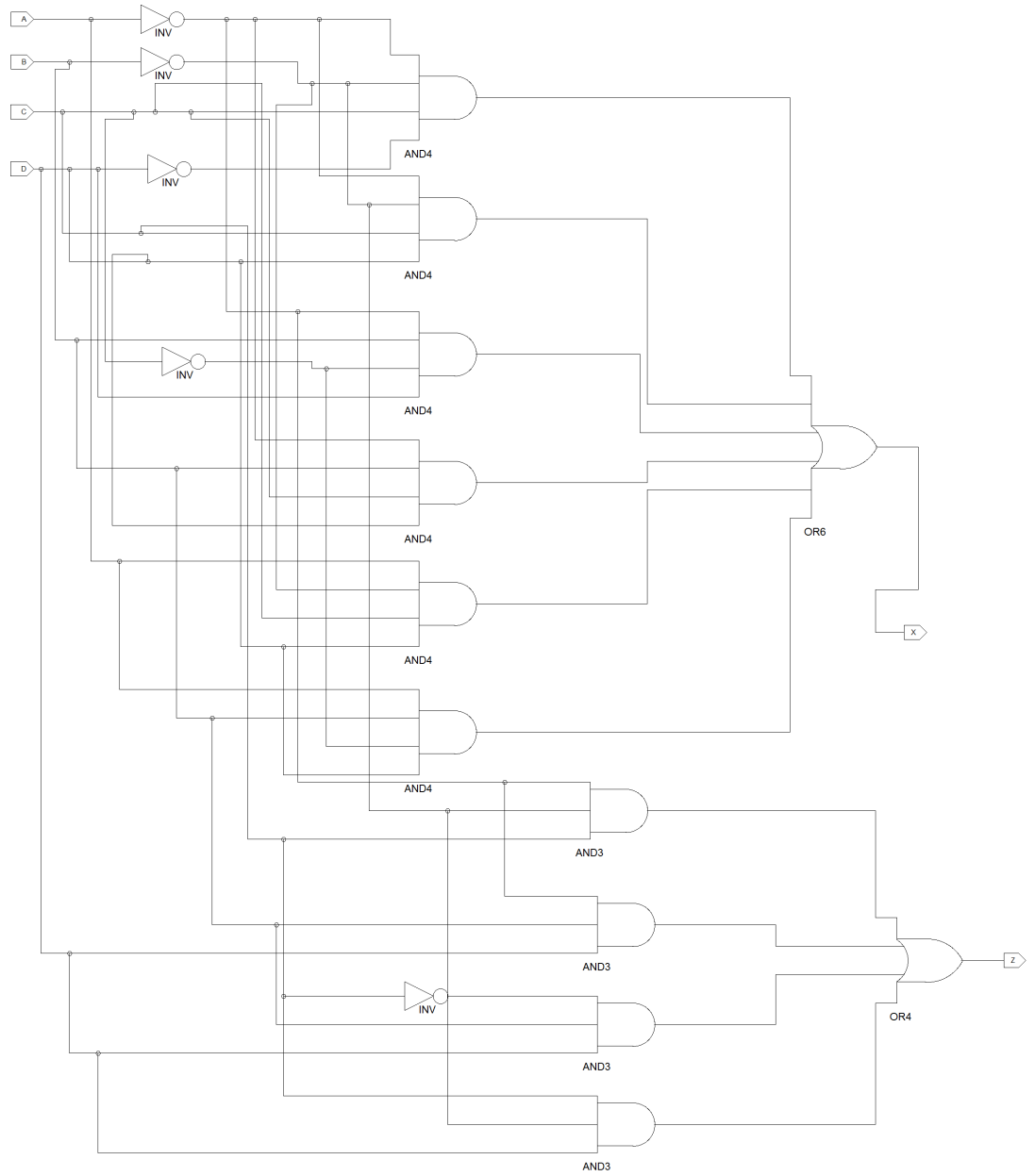- b. **Introduction.** This lab involves using logic gates to determine if a four bit unsigned number is a prime.
- c. **Project Description.** The four bits of the number are mapped to four inputs A , B , C and D . If the number represented by the bits is true, then the output is 1; otherwise, it is 0. A Karnaugh map is used to simplify the equation and both the simplified and unsimplified equations are simultaneously tested using the Diligent board.
- d. **Schematic.**



Truth Table.

A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

Karnaugh Map.

Using Karnaugh map, we have that

	00	01	11	10
00	0	0	1	1
01	0	1	1	0
11	0	1	0	0
10	0	0	1	0

so that $X(A, B, C, D) = \overline{A}BC + \overline{A}BD + B\overline{C}D + \overline{B}CD$.